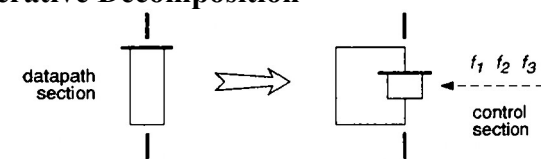
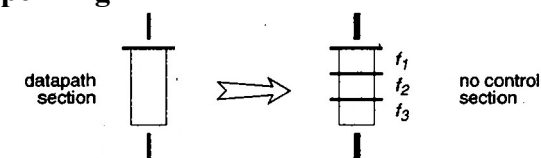
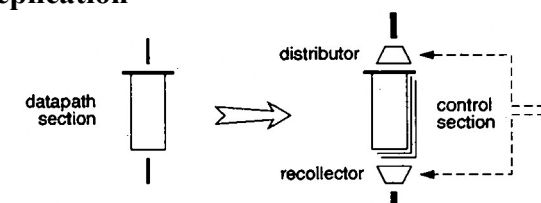
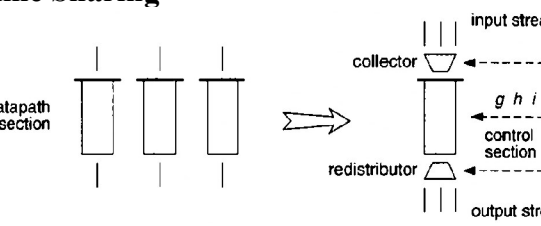
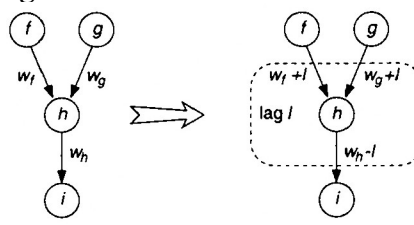



VLSI I – Short Summary

by Stephan Senn, D-ITET

Universal Transformations

| | |
|--|---|
| <p>Iterative Decomposition</p>  <p>d: level of decomposition</p> | $\frac{A_f}{d} + A_{reg} \leq A(d) \leq A_f + A_{reg} \quad , \quad L(d) = d$ $cpd(d) = d \quad , \quad t_{lp}(d) = \frac{t_f}{d} + t_{reg} \quad , \quad T(d) = d \cdot t_{lp}(d)$ $E_f + d E_{reg} < E(d)$ $d A_{reg} t_{reg} + A_{reg} t_f + A_f t_{reg} + \frac{1}{d} A_f t_f \leq AT(s)$ $AT(d) \leq d(A_f + A_{reg})t_{reg} + (A_f + A_{reg})t_f$ |
| <p>Pipelining</p>  <p>p: pipeline stages</p> | $A(p) = A_f + p A_{reg} \quad , \quad L(p) = p \quad , \quad cpd(p) = 1$ $t_{lp}(p) = \frac{t_f}{p} + t_{reg} \quad , \quad T(p) = 1 \cdot t_{lp}(p)$ $AT(p) = p A_{reg} t_{reg} + A_{reg} t_f + A_f t_{reg} + \frac{1}{p} A_f t_f$ $E(p) = E_f + p E_{reg}$ |
| <p>Replication</p>  <p>q: number of replicated items</p> | $A(q) = q(A_f + A_{reg}) \quad , \quad L(q) = 1 \quad , \quad cpd(q) = \frac{1}{q}$ $t_{lp}(q) = t_f + t_{reg} \quad , \quad T(q) = \frac{1}{q} \cdot t_{lp}(q)$ $AT(q) = (A_f + A_{reg})(t_f + t_{reg}) \quad , \quad E(q) = E_f + E_{reg}$ |
| <p>Time Sharing</p>  <p>s: number of shared resources</p> | $\max(A_f) = (A_g, A_h, A_i) \quad , \quad \max(t_f) = (t_g, t_h, t_i)$ $\sum A_f = (A_g + A_h + A_i) \quad , \quad \sum E_f = (E_g + E_h + E_i)$ $\max(A_f) + A_{reg} \leq \sum A_f + A_{reg}$ $L(s) = s \quad , \quad cpd(s) = s \quad , \quad t_{lp}(s) = \max(t_f) + t_{reg}$ $T(s) = s \cdot t_{lp}(s)$ $s[\max(A_f) + A_{reg}][\max(t_f) + t_{reg}] \leq AT(s)$ $AT(s) \leq s[\sum A_f + A_{reg}][\max(t_f) + t_{reg}]$ $s \max(E_f) + E_{reg} \leq E(s)$ |
| <p>Retiming</p>  | <p>The parameters A, t, L, cpd and E don't change.</p> <p>The longest path t_{lp} is shortened!</p> |

Discrete Timed Event-Driven Simulation

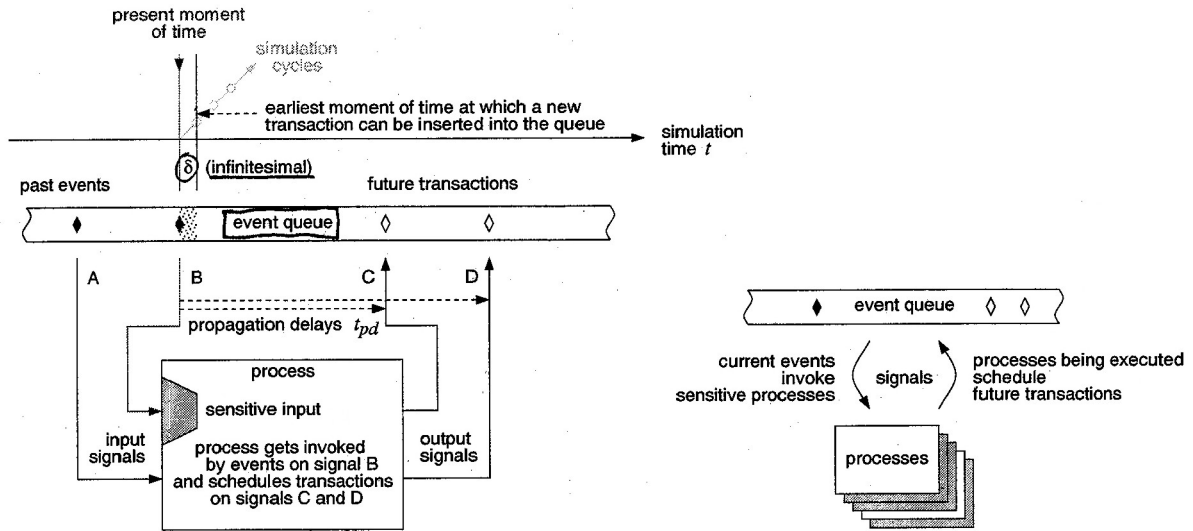


Design Parameters

- Circuit Size : A
- Latency : L
- Cycles per Data Item : cpd
- Computation Period : T_{cp}
- Longest Path Length : $t_{lp} \leq T_{cp}$
- Computation Rate : $f_{cp} = \frac{1}{T_{cp}}$
- Time per Data Item : $T = cpd \cdot T_{cp} \geq cpd \cdot t_{lp}$
- Data Throughput : $\Theta = \frac{1}{T}$
- Size-Time Product : $AT = \frac{A}{\Theta}$
- Energy per Data Item : $E = PT = \frac{P}{\Theta}$
- Power-Delay Product : $pdp = P \cdot t_{lp}$
- Clock Period : $T_{clk} (=T_{cp} \text{ if single-edge triggered})$


Timing

Combinational Logic, Flip-Flop and Latches



a) Combinational Logic

 


b) Flip-Flop

 



positive edge triggered

  





c) Latch

 

passes while high holds while low

  

Anceau Diagram and FSM-Timing Scheme

  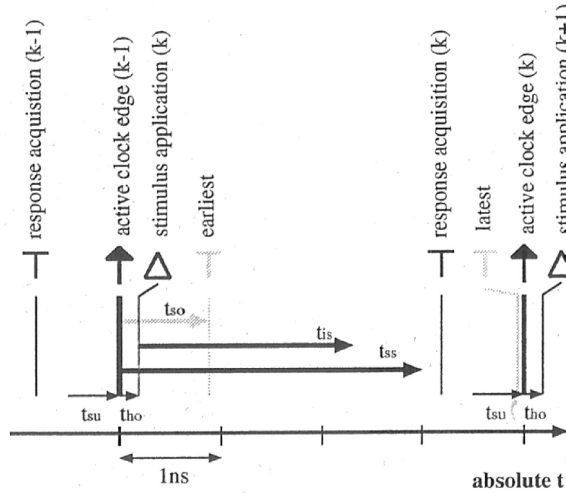 

- events:
- ▲ active clock edge
 - △ stimulus application
 - ⊥ response acquisition

Hold-Time Condition:

$$t_{ho} (+ t_{hi}) < t_{cd} + t_{cd,d} \quad t_{hi}: \text{high-time of a latch}$$

Timing of a System:

$$t_{su,sys} = -t_{d,clk} + t_{su,ff} + t_{cd,comb} \quad t_{d,clk}: \text{clock delay}$$

$$t_{ho,sys} = t_{d,clk} + t_{ho,ff} - t_{cd,comb}$$

$$t_{pd,sys} = t_{d,clk} + t_{pd,ff} + t_{pd,comb}$$

$$t_{cd,sys} = t_{d,clk} + t_{cd,ff} + t_{cd,comb}$$

Sign-Rule for Setup- and Hold-Time:

- Setup-Time: + ←
- Hold-Time: → +


Finite State Machines

| | | |
|---|--|--|
| <p>Mealy</p> <p>$s(k+1) = f(i(k), s(k))$ $o(k) = g(i(k), s(k))$</p> | <p>Moore</p> <p>$s(k+1) = f(i(k), s(k))$ $o(k) = g(s(k))$</p> | <p>Medwedjew</p> <p>$s(k+1) = f(i(k), s(k))$ $o(k) = s(k)$</p> |
| <p>Others:</p> | | |
| <p>Autonomous Automata</p> <p>$s(k+1) = f(s(k))$, no input! $o(k) = g(s(k))$</p> | <p>Delay Automata</p> <p>$s(k+1) = f(i(k))$ $o(k) = g(s(k))$</p> | <p>Combinational Logic</p> <p>$o(k) = g(i(k))$, no states!</p> |

VHDL Code Fragments

Flip-Flop
 
```
-- updating of state
-- sensitivity list, no more signals accepted!
memzing : process (CLOCK, RESET) is
begin
-- no other statement allowed here!
```



```

-- activities triggered by asynchronous active-high reset
if RESET = '1' then
    PRESENTSTATE <= STARTSTATE;
    ...
-- activities triggered by rising edge of clock
elsif CLOCK'event and CLOCK='1' then -- no more term allowed here!
    -- extra subconditions, if any, accepted here.
    PRESENTSTATE <= NEXTSTATE;
    ...
end if;
-- no more statement allowed here!
end process memzing;

```

Mealy and Moore FSM

```

memless : process (INPxD, STATExDP) is
begin
STATExDN <= STATExDP; -- remain in present state
case STATExDP is
when st0 => -- state in a Mealy FSM
    if INPxD = <in1> then OUPxD <= <out1>;
    elsif INPxD = <in2> then STATExDN <= <next_statel>;
    ...
    else OUPxD <= <out>; -- catch parasitic input!
    end if;
when st1 => -- state in a Moore FSM
    if INPxD = <in1> then STATExDN <= <next_statel>;
    elsif INPxD = <in2> then STATExDN <= <next_state2>;
    ...
    else STATExDN <= <state> -- catch parasitic input!
    end if;
    OUPxD <= <out1>;
    ...
when others => -- tie up parasitic states for synthesis!
end case;
end process memless;

```

What makes an Algorithm suitable for dedicated VLSI Architectures?

- | | |
|--|--|
| <ul style="list-style-type: none"> • Loose coupling between major processing tasks • Simple control flow • Regular data flow • Reasonable storage requirements • Compatible with finite precision arithmetics • Non-recursive linear time-invariant computation • No transcendental functions | <ul style="list-style-type: none"> • No divisions and multiplications on wide data words • One argument fixed in computationally expensive operations • Throughput rather than latency is what matters • Simple initialization |
|--|--|